

CS-301

ANALOG AND DIGITAL ELECTRONICS

Time Allotted: 3 Hours

Full Marks: 70

The questions are of equal value.

The figures in the margin indicate full marks.


Candidates are required to give their answers in their own words as far as practicable.

GROUP A
(Multiple Choice Type Questions)

1. Answer any *ten* questions. 10×1 = 10
- (i) What is Gray equivalent of the binary 1101?
(A) 1101 (B) 1011
(C) 0111 (D) none of these
- (ii) A 2-transistor class-B amplifier is usually called
(A) dual amplifier (B) inverting amplifier
(C) symmetrical amplifier (D) push-pull amplifier
- (iii) The gain of an amplifier in general is
(A) imaginary (B) complex
(C) real (D) none of these
- (iv) For critical modulation the value of modulation index is
(A) 0.5 (B) 1
(C) 0.75 (D) 0.1

- (v) Schmitt trigger generates
- (A) triangular wave
 - (B) square wave
 - (C) saw tooth wave
 - (D) none of these
- (vi) A Wien bridge oscillator has a frequency
- (A) $1/2\pi\sqrt{RC}$
 - (B) $1/\sqrt{RC}$
 - (C) $1/2\pi(RC)$
 - (D) none of these
- (vii) The Q point in a voltage amplifier is selected in the middle of the active region because
- (A) it gives better stability
 - (B) the biasing circuit then needs less number of resistors
 - (C) the circuit needs a small d.c. voltage
 - (D) it gives a distortion less output
- (viii) Astable Multivibrator may be used as
- (A) frequency to voltage converter
 - (B) squaring circuit
 - (C) voltage to frequency converter
 - (D) comparator circuit
- (ix) Which one of the following is a reflected code?
- (A) 8421 code
 - (B) excess-3 code
 - (C) Gray code
 - (D) ASCII code
- (x) The value of base X for which $(211)_X = (0.52)_8$ is
- (A) 08
 - (B) 10
 - (C) 16
 - (D) 07
- (xi) The minimum number of flip-flop require to design a MOD-10 counter is
- (A) 03
 - (B) 10
 - (C) 04
 - (D) 05

(xii) The output voltage of the circuit

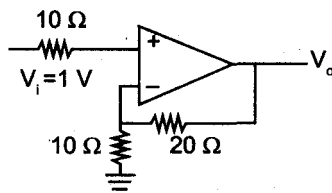

- (A) 0 V (B) 1 V
(C) 2 V (D) 3 V

GROUP B
(Short Answer Type Questions)

Answer any *three* questions.

3×5 = 15

2. Simplify the following expression using a K-Map and realize the simplified expression using NAND gates only:
 $G(A, B, C, D) = \Sigma(1, 2, 3, 5, 6, 11, 12) + d(7, 8, 10, 14)$
3. Implement a full adder circuit using a 3-to-8 decoder and other logic gates.
4. What is the basic principle of oscillation? What is Barkhausen criterion?
5. Implement a clocked JK flip-flop using NAND gates only.
6. What are the advantages of push-pull amplifier? Why the push-pull circuit is called so?

GROUP C
(Long Answer Type Questions)

Answer any *three* questions.

3×15 = 45

7. (a) Design an asynchronous 4-bit up-down counter and it will count up when a signal line $M = 0$ and count down when a signal line $M = 1$. Use only JK flip-flops and EX-OR gates. 15
8. What is the difference between a combinational and a sequential circuit? Write down the excitation table of J-K and T flip flop. Derive their Boolean expression for the characteristic equations. What is a counter? Draw the circuit diagram and output waveform of a mod 6 ripplecounter. 15
9. A 10 stage ripple counter is constructed using individual flip flops, each having a delay of 5 ns. What is the maximum allowable frequency of the counter which will still allow correct reading? 15
- 10.(a) Explain the operation of a R-2R Ladder type DAC with circuit diagram. 7
(b) Explain the working of a successive approximation register type ADC. 8
11. Write short notes on any *three* of the following: 3×5
 - (a) Serial input parallel output shift register
 - (b) 8:3 encoder
 - (c) Parity generator
 - (d) Ring counter
 - (e) Voltage comparator using Op-Amp